
# Pipelined CPU Lab 8 Report

Ruben Carbajal Claire Cropper

#### Waveform:

 

## **Testbench:**

```
Instruction = 32'b100011 00000 00110 0000000000001000; // LW $R6, 8(R0)
#10;
Instruction = 32'b000000 00110 00011 01001 00000 100101; //or $R9, $R6, $R3 1 ahead hazard
Instruction = 32'b000000_00001_00010_01000_00000_100010; //sub $R8, $R1, $R2
#10:
Instruction = 32'b000000_00101_01001_01010_00000_100000; //add $R10, $R5, $R9
#10;
Instruction = 32'b101011 00000 00111 000000000001100; // SW $R7, 12(R0)
#10;
Instruction = 32'b001000 01010 01011 0000000000111001; //addi $R11, $R10, 57 2 ahead hazard
#10;
Instruction = 32'b000000 00111 00010 01100 00000 100100; //and $R12, $R7, $R2
#10;
Instruction = 32'b000000_00100_01100_01101_00000_100100; //and $R13, $R4, $R12 1 ahead hazard
#10;
Instruction = 32'b000000_01011_01100_01101_00000_101010; //slt $R13, $R11, $R12
Instruction = 32'b100011_00000_01110_000000000010000; // LW $R14, 16(R0)
Instruction = 32'b101011_00010_01110_000000000000000; // SW $R14, 0(R2) RAW hazard
#10;
```

For the testbench, we used the provided code and then added 3 additional instructions to show two 1-ahead hazards and one 2-ahead hazard. The testbench includes 4 types of hazards that our hazard flag detects creates the appropriate stall as seen in PC Out.


## 1-ahead Hazard:

In order to detect a 1-ahead hazard, in our hazardunit.v module we compared IDEX\_Rd to IDEX\_Rs and IDEX\_Rt, and depending on if either of those conditions were true, in conjunction with inWex and IDEX\_Rd != 0, it would modify IFIDWrite, PCWrite, and HazardMux to stall the pipeline 1 cycle. This part compares the control signals from stage 1 to stage 2 of the pipeline.

## 2-ahead Hazard:

In order to detect a 2-ahead hazard, in our hazardunit.v module we compared EXMEM\_Rd to IDEX\_Rs and IDEX\_Rt, and depending on if either of those conditions were true, in conjunction with inWmem and when EXMEM\_Rd != 0, it would modify IFIDWrite, PCWrite, and HazardMux to stall the pipeline 2 cycles. This part compares the control signals from stage 1 to stage 3 of the pipeline.

## **Schematic:**

 

This schematic as provided by the Discussion slides aided our understanding of the appropriate control signals and wires.